
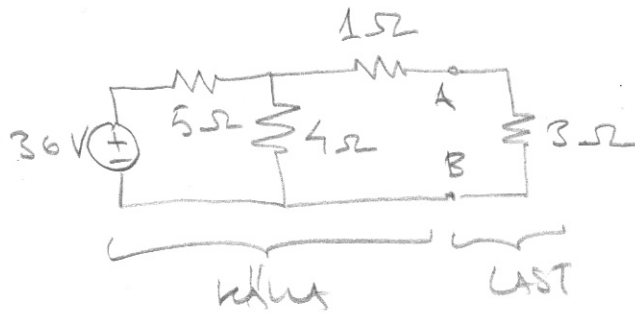


3.51)

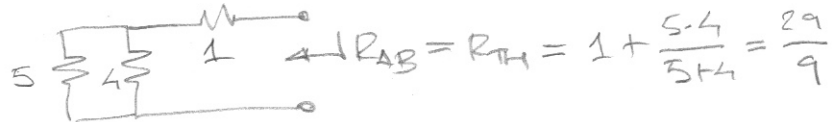

Beskrivna Thvenin-
EKVIVALENTEN
KRETSEN.

Lösning = Beskriv R_{TH}



Därefter V_{TH}



$$V_i \text{ för } i = \frac{36}{5+4} = 4 \text{ A}$$

$$\text{och } V_{TH} = 4 \cdot 4 = 16 \text{ V}$$

Då får vi Thvenin EKVIVALENTEN



$$\underline{\text{Svar}} = \begin{cases} R_{TH} = \frac{29}{9} \Omega \\ V_{TH} = 16 \text{ volt} \end{cases}$$